

# **Thapar Institute of Engineering and Technology**



**THAPAR INSTITUTE**  
OF ENGINEERING & TECHNOLOGY  
(Deemed to be University)

## **Embedded Systems (Verilog Programming)**

**Submitted by: COE 4**

**Submitted to: Ms. Gaganpreet Kaur**

# INDEX

<b>S No.</b>	<b>Experiment</b>	<b>Page</b>
1	Write a verilog program to show the outputs of AND, OR, XOR, NAND, NOR, XNOR and NOT gates	2
2	a). Write a verilog program to show the output of Half adder. b). Write a verilog program to show the output of full adder.	4
3	a). Write a verilog program to show the output of Half subtractor. b). Write a verilog program to show the output of full subtractor.	8
4	Write a program for 4x2 encoder using case statement. Verify the logic using truth table and time wave	12
5	Write a program for 2*1 MUX using conditional operator. Verify logic using truth table and time wave	14
6	Write a program for 1x4 DEMUX using conditional operator. Verify logic using truth table and time wave	16
7	a).Write a verilog program to show the output of T flip-flop b)..Write a verilog program to show the output of JK flip-flop	20

**Q1. Write a verilog program to show the outputs of AND, OR, XOR, NAND, NOR, XNOR and NOT gates.**

**Ans.**

```
module m1(A,B,C,D,E,F,G,H,I);
input A,B;
output C,D,E, F, G, H, I;
assign C= A&B;
assign D= A|B;
assign E= A^B;
assign F= ~(A&B);
assign G= ~(A|B);
assign H= ~(A^B);
assign I= ~A;
endmodule

module test;
reg a,b;
wire c,d,e,f,g,h,i;
m1 g1(a,b,c,d,e,f,g,h,i);
initial
begin
$dumpfile("first.vcd");
$dumpvars(0,test);
$display("a\tb\tAND\tOR\tXOR\tNAND\tNOR\tXNOR\tNOT(A)");
$monitor("%b\t%b\t%b\t%b\t%b\t%b\t%b\t%b\t%b",a,b,c,d,e,f,g,h,i);
a=0;b=0;
#10 a=0;b=1;
#10 a=1;b=0;
#10 a=1;b=1;
#10
$finish;
end
endmodule
```


```
Command Prompt - gtkwave first.vcd

g:\IMPORTANT\Old Laptop\Thapar\Sem 6\Embedded Systems>iverilog hello.v
g:\IMPORTANT\Old Laptop\Thapar\Sem 6\Embedded Systems>vvp a.out
Hello Everyone
VCD info: dumpfile first.vcd opened for output.
a      b      AND      OR      XOR      NAND      NOR      XNOR      NOT(A)
0      0      0      0      0      1      1      1      1
0      1      0      1      1      1      0      0      1
1      0      0      1      1      1      0      0      0
1      1      1      1      0      0      0      1      0

g:\IMPORTANT\Old Laptop\Thapar\Sem 6\Embedded Systems>gtkwave first.vcd
GTKWave Analyzer v3.3.71 (w)1999-2016 BSI

[0] start time.
[40] end time.
```

Command Prompt

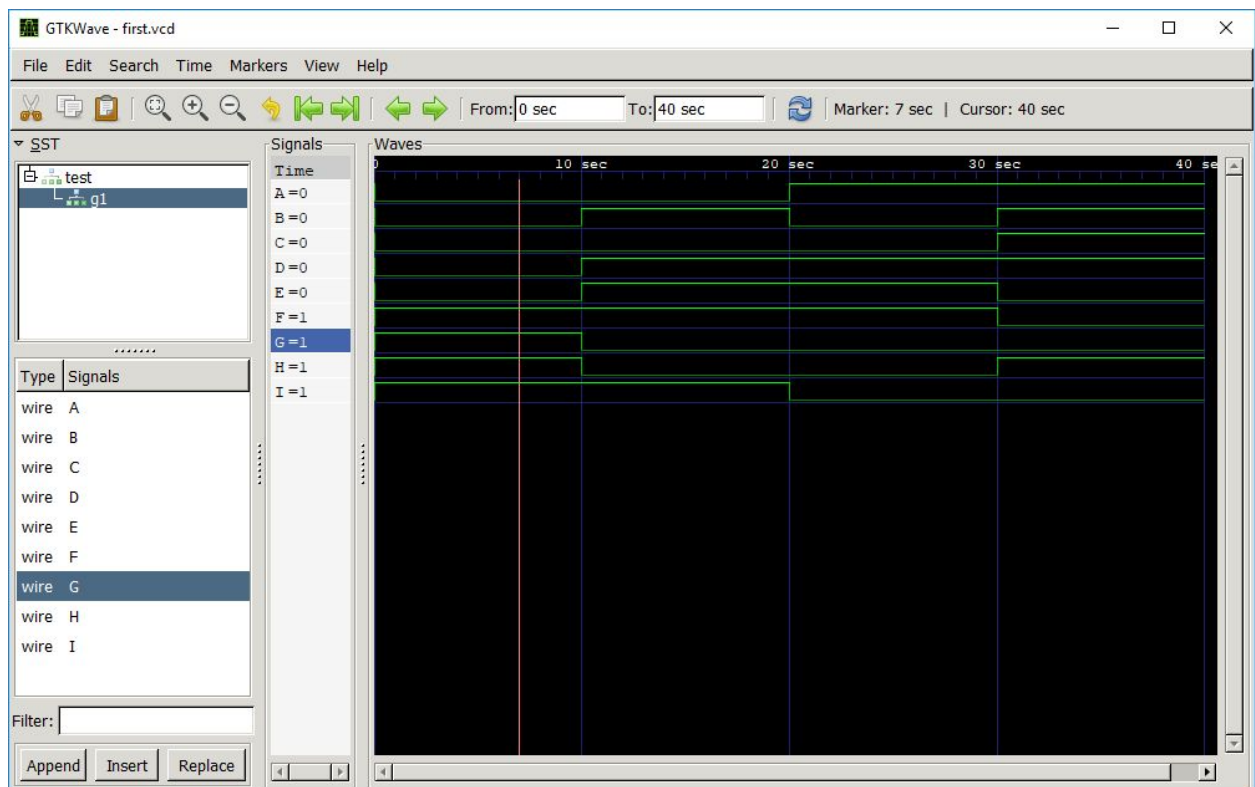

GTK Wave

**Q2(a). Write a verilog program to show the output of Half adder.**

**Ans.**

```
module halfadder(a,b,carry,sum);
input a,b;
output carry,sum;
assign carry=a&b;
assign sum=a^b;
endmodule


module test;
reg a1,b1;
wire carry1,sum1;
halfadder h1(a1,b1,carry1,sum1);
initial
begin
$dumpfile("dump1.vcd");
$dumpvars(0,test);
$display("a\tb\tcarry\tsum");
$monitor("%b\t%b\t%b\t%b",a1,b1,carry1,sum1);
a1=0;
b1=0;
#10;
a1=0;
b1=1;
#10;
a1=1;
b1=0;
#10;
a1=1;
b1=1;
#10;
$finish;
end
endmodule
```

```

[CSED@localdomain ~]$ iverilog halfadder.v
[CSED@localdomain ~]$ vvp a.out
a          b          carry    sum
0          0          0         0
0          1          0         1
1          0          0         1
1          1          1         0

```

Command Prompt

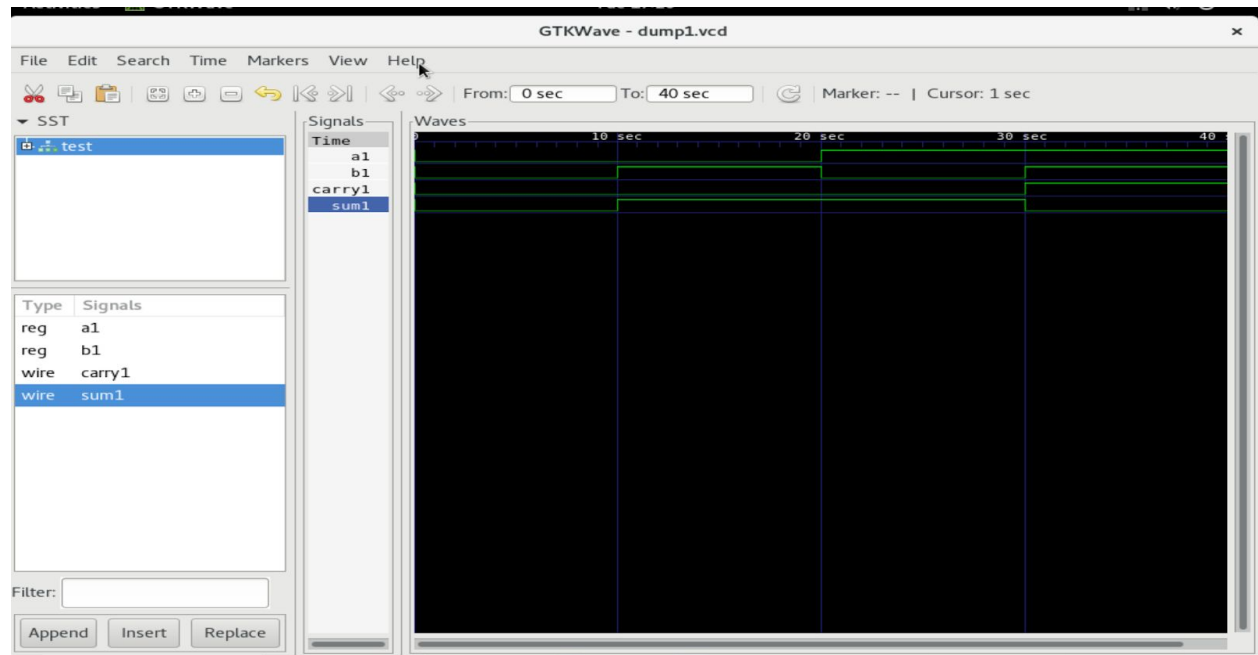

GTK Wave

**Q2(b). Write a verilog program to show the output of Full adder.**

**Ans.**

```
module fulladder(a,b,c,carry,sum);
input a,b,c;
output carry,sum;
assign carry=a&b|a&c|b&c;
assign sum=a^b^c;
endmodule


module test;
reg a1,b1,c1;
wire carry1,sum1;
fulladder h1(a1,b1,c1,carry1,sum1);
initial
begin
$dumpfile("dump1.vcd");
$dumppvars(0,test);
$display("a\tb\tc\tcarry\tsum");
$monitor("%b\t%b\t%b\t%b\t%b",a1,b1,c1,carry1,sum1);
a1=0;b1=0;
c1=0;#10;
a1=0;b1=0;
c1=1;#10;
a1=0;b1=1;
c1=0;#10;
a1=0;b1=1;
c1=1;#10;
a1=1;b1=0;
c1=0;#10;
a1=1;b1=0;
c1=1;#10;
a1=1;b1=1;
c1=0;#10;
a1=1;b1=1;
c1=1;#10;
$finish;
end
endmodule
```

```

[CS@localdomain ~]$ iverilog fulladder.v
[CS@localdomain ~]$ vvp a.out
VCD info: dumpfile dump1.vcd opened for output.
a      b      c      carry  sum
0      0      0      0      0
0      0      1      0      1
0      1      0      0      1
0      1      1      1      0
1      0      0      0      1
1      0      1      1      0
1      1      0      1      0
1      1      1      1      1
[CS@localdomain ~]$

```

Command Prompt

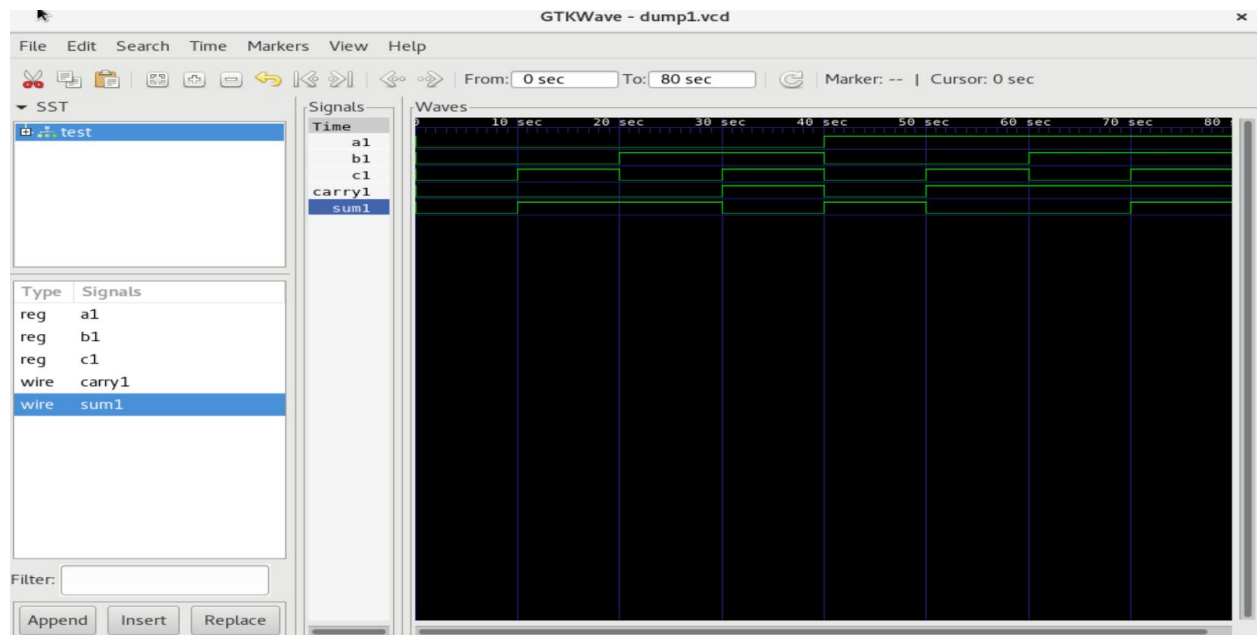

GTK Wave



**Q3(a). Write a verilog program to show the output of Half subtractor.**


**Ans:**

```
module halfsubtractor(x,y,d,b);
input x,y;
output d,b;
assign d=x^y;
assign b=~x&y;
endmodule

module test;
reg x1,y1;
wires s1,c1;
halfsub g1(x1,y1,d1,b1);
initial
begin
$dumpfile("dump1.vcd");
$dumpvars(0,test);
$display("x y d b");
$monitor("%b\t%b\t%b\t%b",x1,y1,s1,c1);
x1=0;
y1=0;
#10 x1=0; y1=0;
#10 x1=0; y1=1;
#10 x1=1; y1=0;
#10 x1=1; y1=1;
#10
$finish;
end
endmodule
```

```
[CSED@localdomain ~]$ iverilog halfsub.v
[CSED@localdomain ~]$ vvp a.out
VCD info: dumpfile dump1.vcd opened for output.
a      b      diff      borrow
0      0      0      0
0      1      1      1
1      0      1      0
1      1      0      0
```

Command prompt

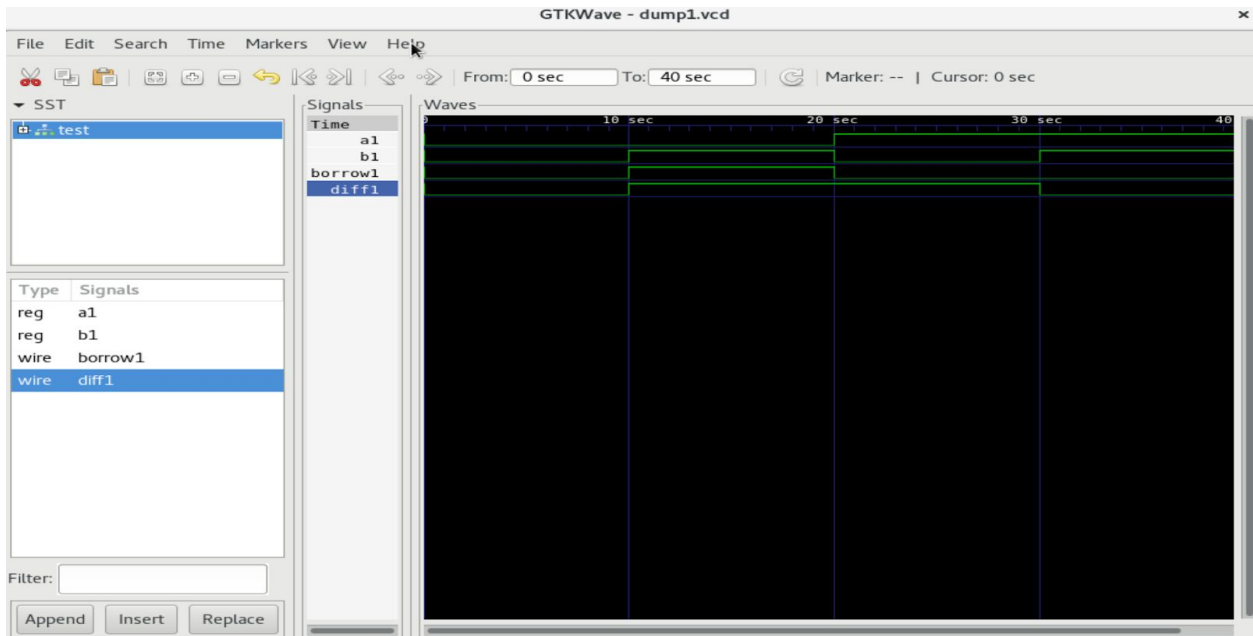

GTK Wave

**Q3(b). Write a verilog program to show the output of Full subtractor.**


**Ans:**

```
module fullsubtractor(x,y,z,d,b);
input x,y,z;
output d,b;
assign d=x^y^z;
assign b=~x&z|~x&y|y&z;
endmodule

Module test;
reg x1,y1,z1;
wire s1,c1;
fullsub g1(x1,y1,z1,s1,c1);
initial
begin
$dumpfile("dump1.vcd");
$dumpvars(0,test);
$display("x y z d b");
$monitor("%b\t%b\t%b\t%b\t%b",x1,y1,z1,s1,c1);
x1=0;
y1=0;
z1=0;
#10 x1=0; y1=0; z1=0;
#10 x1=0; y1=0; z1=1;
#10 x1=0; y1=1; z1=0;
#10 x1=0; y1=1; z1=1;
#10 x1=1; y1=0; z1=0;
#10 x1=1; y1=0; z1=1;
#10 x1=1; y1=1; z1=0;
#10 x1=1; y1=1; z1=1;
#10
$finish;
end
endmodule
```

```
CSED@localdomain:~  
File Edit View Search Terminal Help  
[CSED@localdomain ~]$ iverilog fullsub.v  
[CSED@localdomain ~]$ vvp a.out  
VCD info: dumpfile dump1.vcd opened for output.  
x y z d b  
0 0 0 0 0  
0 0 1 1 1  
0 1 0 1 1  
0 1 1 0 1  
1 0 0 1 0  
1 0 1 0 0  
1 1 0 0 0  
1 1 1 1 1  
[CSED@localdomain ~]$ gtkwave dump1.vcd
```

Command prompt

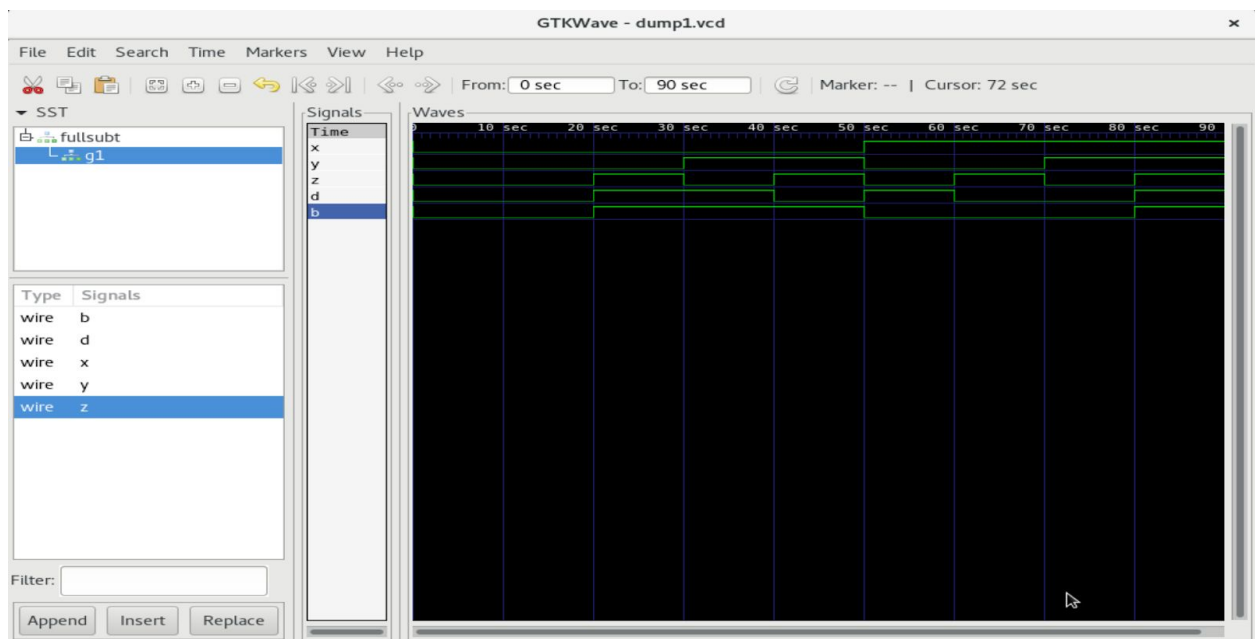


GTK Wave

**Q.4 Write a program for 4x2 encoder using case statement. Verify the logic using truth table and time wave.**

```
Ans. module enc(in, out);
    input [3:0] in;
    output [1:0] out;
    reg [1:0] out;
    always @(*)
    begin
        case(in)
            4'b0001:
                out=2'b00;
            4'b0010:
                out=2'b01;
            4'b0100:
                out=2'b10;
            4'b1000:
                out=2'b11;
        endcase
    end
endmodule

module test;
    reg [3:0] in;
    wire [1:0] out;
    enc e(in,out);
    initial
    begin
        $dumpfile("dump.vcd");
        $dumpvars(0,test);
        $display("in3\tin2\tin0\tinO\tto1\tto0");
        $monitor("%b\t%b\t%b\t%b\t%b\t%b",in[3],in[2],in[1],in[0],out[1],out[0]);

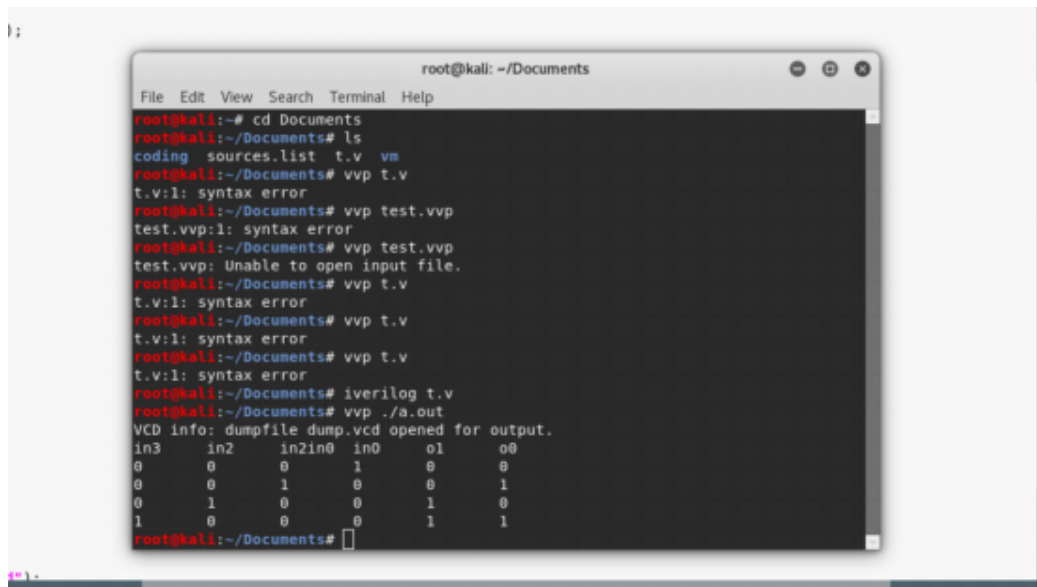
        in=4'b0001;
        #10
        in=4'b0010;
        #10
        in=4'b0100;
        #10
        in=4'b1000;
        #10 $finish;
    end
endmodule
```



A terminal window titled "root@kali: ~/Documents" showing the following commands and output:

```
root@kali:~# cd Documents
root@kali:~/Documents# ls
coding sources.list t.v vm
root@kali:~/Documents# vvp t.v
t.v:1: syntax error
root@kali:~/Documents# vvp test.vvp
test.vvp:1: syntax error
root@kali:~/Documents# vvp test.vvp
test.vvp: Unable to open input file.
root@kali:~/Documents# vvp t.v
t.v:1: syntax error
root@kali:~/Documents# vvp t.v
t.v:1: syntax error
root@kali:~/Documents# vvp t.v
t.v:1: syntax error
root@kali:~/Documents# iverilog t.v
root@kali:~/Documents# vvp ./a.out
VCD info: dumpfile dump.vcd opened for output.
in3   in2   in2in0  in0   o1    o0
0     0     0       1     0     0
0     0     1       0     0     1
0     1     0       0     1     0
1     0     0       0     1     1
root@kali:~/Documents#
```

Command Prompt

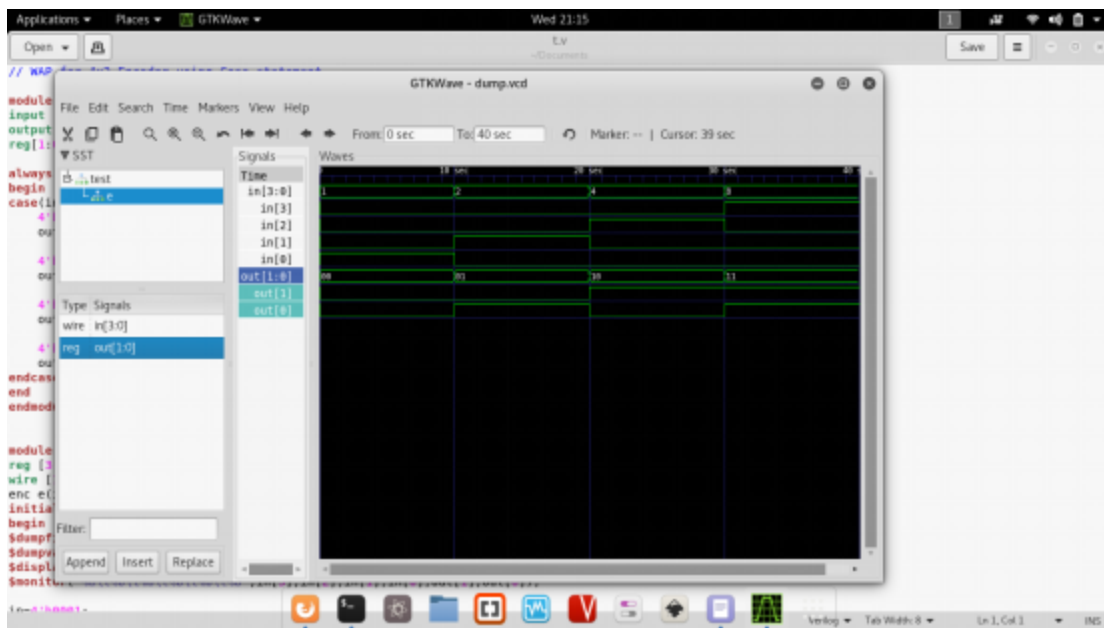

GTK Wave

**Q5. Write a program for 2\*1 MUX using conditional operator. Verify logic using truth table and time wave.**

**Ans.**

```
module m1(C, A, B, D);
input A, B, C;
output D;
assign D=C? B: A;
endmodule

module test2;
reg a, b, c;
wire d;
m1 g1( c, a, b, d);
initial
begin
$dumpfile( "mux.vcd" );
$dumpvars( 0, test2);
$display( "S\tA\tB\tR" );
$monitor( "%b\t%b\t%b\t%b" , c, a, b, d);
a= 0; b= 0; c= 0;
#a= 0; b= 0; c= 1;
#a= 0; b= 1; c= 0;
#a= 0; b= 1; c= 1;
#a= 1; b= 0; c= 0;
#a= 1; b= 0; c= 1;
#a= 1; b= 1; c= 0;
#a= 1; b= 1; c= 1;

#10 $finish;
end
endmodule
```

```


[CS@localhost ~]$ gedit mux.v
[CS@localhost ~]$ iverilog mux.v
[CS@localhost ~]$ ./a.out
VCD info: dumpfile mux.vcd opened for output.
S      A      B      R
0      0      0      0
1      0      0      0
0      0      1      0
1      0      1      1
0      1      0      1
1      1      0      0
0      1      1      1
1      1      1      1
[CS@localhost ~]$ gtkwave mux.vcd

GTKWave Analyzer v3.3.72 (w)1999-2016 BSI

[0] start time.
[80] end time.
WM Destroy

```

Command Prompt

 

GTK Wave



**Q.6) Write a program for 1x4 DEMUX using conditional operator. Verify logic using truth table and time wave**

**Ans.**

```
module demux12(A,S,Y1,Y2,Y3,Y4);
input A;
input[1:0] S;
output Y1,Y2,Y3,Y4;
reg Y1,Y2,Y3,Y4;
always @ (*)
begin
    if(S==2'b00)
    begin
        Y1=A;
        Y2=0;
        Y3=0;
        Y4=0;
    end
    else if(S==2'b01)
    begin
        Y1=0;
        Y2=A;
        Y3=0;
        Y4=0;
    end
    else if(S==2'b10)
    begin
        Y1=0;
        Y2=0;
        Y3=A;
        Y4=0;
    end
    else if(S==2'b11)
    begin
        Y1=0;
        Y2=0;
        Y3=0;
        Y4=A;
    end
end
end
endmodule

module main;
reg A;
```

```

reg [1:0]S;
wire Y1,Y2,Y3,Y4;
demux12 dmxA(A,S,Y1,Y2,Y3,Y4);

initial
begin
$dumpfile( "demux.vcd" );
$dumpvars( 0, main);
$display("A\tS[0]\tS[1]\tY1\tY2\tY3\tY4");
$monitor("%b\t%b\t%b\t%b\t%b\t%b\t%b",A,S[0],S[1],Y1,Y2,Y3,Y4);

A=0;
S=2'b00;
#10 S=2'b01;
#10 S=2'b10;
#10 S=2'b11;

A=1;
S=2'b00;
#10 S=2'b01;
#10 S=2'b10;
#10 S=2'b11;
$finish;
end
endmodule


```

```
Command Prompt - gtkwave demux.vcd

C:\iverilog>iverilog 3071_demux.v
C:\iverilog>vvp a.out
VCD info: dumpfile demux.vcd opened for output.
# S[0] S[1] Y1 Y2 Y3 Y4
0 0 0 0 0 0
0 1 0 0 0 0
0 0 1 0 0 0
1 0 0 1 0 0
1 1 0 0 1 0
1 0 1 0 1 0
1 1 1 0 0 1
#
C:\iverilog>gtkwave demux.vcd

GTKWave Analyzer v3.3.71 (w)1999-2016 BSI
[0] start time.
[60] end time.
-
```

Command Prompt

 

GTK Wave

**Q.7(a) .Write a verilog program to show the output of T flip-flop.**

**Ans-**

```
module mytff(t,q,qb,clk);
input  t,clk;
output q,qb;
reg q,qb;
initial q=0;
always@(posedge clk)
begin
    if (t==1)
    begin
        q=~q;
    end
    Else
        begin
            q=q;
        end
        qb=~q;
    end
endmodule

module tff_tb;
reg a,b;
wire y,yb;
mytff out(.t(a), .clk(b),.q(y),.qb(yb));
initial
begin
    $dumpfile("dumpu.vcd");
    $dumpvars(0,tff_tb);
    $display("a0\tb0\ty0\tyb0");
    $monitor("a=%d,b=%d,y=%d,yb=%d,\n",a,b,y,yb);
    a=0;
    b=0;
    #100;
    b=1;
    #100;
    a=1;
    b=0;
    #100;
    b=1;
    #100;
```

```
end
endmodule
```

```
C:\Users\Intra Pc>iverilog mytff.v

C:\Users\Intra Pc>vvp a.out
VCD info: dumpfile dumpu.vcd opened for output.
a0      b0      y0      yb0
a=0,b=0,y=0,yb=x,
a=0,b=1,y=0,yb=1,
a=1,b=0,y=0,yb=1,
a=1,b=1,y=1,yb=0,


C:\Users\Intra Pc>gtkwave dumpu.vcd

GTKWave Analyzer v3.3.66 (w)1999-2015 BSI

[0] start time.
[400] end time.
WM Destroy

C:\Users\Intra Pc>
```

Command prompt

 

## GTK Wave

**Q.7(b) Write a verilog program to show the output of JK FlipFlop**

**Ans.** module jkff(input [1:0] jk,input clk,output q,output qb);

```
reg q,qb;
always@(posedge clk)
begin
case(jk)
2'b00:q=q;
2'b01:q=0;
2'b10:q=1;
2'b11:q=~q;
endcase
qb=~q;
end
endmodule
```

```
module test;
reg [1:0]jk;
reg clk,i;
wire q,qb;
jkff s(jk,clk,q,qb);
initial
begin
$dumpfile("first.vcd");
$dumpvars(1,test);
$display("clk\tjk1\tjk0\tq\t~q");
$monitor("%b\t%b\t%b\t%b\t%b",clk,jk[1],jk[0],q,qb);
jk=2'b00;#10
jk=2'b01;#10
jk=2'b10;#10
jk=2'b11;#10
$finish;
end
initial
begin
clk=0;
for(i=0;i<=20;i++)
#5 clk=~clk;
end
endmodule
```


```
C:\WINDOWS\system32\cmd.exe

C:\Users\hp\Documents>
C:\Users\hp\Documents>
C:\Users\hp\Documents>
C:\Users\hp\Documents>iverilog jkff.v

C:\Users\hp\Documents>vvp a.out
VCD info: dumpfile first.vcd opened for output.
clk      jk1      jk0      q      ~q
0         0         0         x         x
1         0         0         x         x
0         0         1         x         x
1         0         1         0         1
0         1         0         0         1
1         1         0         1         0
0         1         1         1         0
1         1         1         0         1
0         1         1         0         1

C:\Users\hp\Documents>gtkwave first.vcd
```

Command Prompt

 

GTK Wave

